

Discrete Superheterodyne Spectrum Analyzer

Comprehensive Circuit Implementation & LTSpice Simulation Guide

Architecture: Swept Superheterodyne | **RF Range:** 0 to 30 kHz (Audio-to-Ultrasound)
IF Channels: 25 kHz (Ch 2) & 35 kHz (Ch 3) | **Resolution Bandwidth (RBW):** 200 Hz ($Q = 125$ to 175)
Active Parts: TL072 JFET Op-Amps (10 ICs), 2N2222 / 2N3904 NPN BJTs, 1N4148 Diodes, ADS1115 ADC

1. System Signal Chain Architecture

The instrument follows the classic swept superheterodyne architecture. An incoming RF signal is buffered, mixed down to a fixed intermediate frequency (IF) by a swept local oscillator (LO), filtered through high-Q bandpass stages, envelope detected, smoothed via a video bandwidth (VBW) filter, and displayed against the LO sweep ramp (X-axis):

```
[ RF Input ] --> [ Preamp / Attenuator ] --> [ 2N2222 Gilbert Mixer ] --> [ Active IF Filter Bank ]
|
[ X-OUT (Tuning Ramp) ] <-- [ Sawtooth VCO (LO) ] -----■
|
v
[ Y-OUT (Spectrum) ] <-- [ Video BW Filter ] <-- [ Envelope Detector ]
```

2. Block-by-Block Circuit Specifications

Block 1: RF Input Preamp & Attenuator (01_RF_Frontend.asc)

- Function:** High input impedance buffer (1 M Ω) with selectable gain (1x, 10x / +20 dB) to condition weak audio signals (10 mV to 1 Vrms) to optimal mixer level (0.5 to 1.0 Vpp).
- Components:** TL072 JFET op-amp ($\pm 9V$ to $\pm 12V$ rails), $C_{in} = 1.0 \mu F$, $R_{in} = 100 \Omega$, $R_{bias} = 1.0 M\Omega$, $R_f = 9.0 k\Omega$, $R_g = 1.0 k\Omega$, $C_{out} = 1.0 \mu F$.

Block 2: Discrete Gilbert Cell Four-Quadrant Mixer (02_Gilbert_Mixer.asc)

- Topology:** 6-transistor active Gilbert cell using 2N2222 BJTs. Driven by single-ended RF and differential LO.
- Bias Network (+12V rail):** $R_1=3.3k$, $R_2=2.2k$, $R_4=2.2k$, $R_3=1.5k$; Base resistors $R_8..R_{11}$, $R_6 = 10 k\Omega$; Tail resistor $R_5 = 390 \Omega$; Collector loads $R_{12}=R_7=2.2 k\Omega$.
- Coupling Capacitors:** Bypass C_1 , C_2 , $C_3 = 10 \mu F$ electrolytic; LO coupling C_4 , $C_5 = 100 nF$; Output $C_{out} = 1.0 \mu F$.

Block 3: IF Active Bandpass Filter Bank (03_IF_Filter_Bank.asc)

- Channel 2 (25 kHz Sallen-Key):** $f_0 = 25,000$ Hz, $BW = 200$ Hz ($Q = 125$). TL072 op-amps, $R_3=R_5=796 k\Omega$ (1%), $R_4=6.34 k\Omega$ (1%), $C_3=C_4=1.0 nF$ (C0G). Includes input divider (10k / 2.2k, -15 dB) to prevent passband clipping.
- Channel 3 (35 kHz MFB Filter Redesign):** $f_0 = 35,000$ Hz, $BW = 200$ Hz ($Q = 175$, $A_v = 2.0$). Replaced oscillating Sallen-Key with Multiple Feedback (MFB) topology. Components: $C_1=C_2=1.0 nF$, R_3 (feedback) = 1.591 M Ω , R_1 (input) = 397.8 k Ω , R_2 (ground) = 12.98 Ω .

Block 4: Diode Envelope Detector & Buffer (04_Envelope_Detector.asc)

- Components:** 1N4148 fast rectifier diode, $C = 10 nF$ reservoir cap, $R = 22 k\Omega$ discharge resistor ($\tau = 220 \mu s$). TL072 unity-gain buffer.

Block 5: Video Bandwidth (VBW) Low-Pass Filter (05_VBW_Filter.asc)

- **Selectable Modes:** Low ($f_c = 50$ Hz, $R = 33k$, $C = 100n$), Medium ($f_c = 200$ Hz, $R = 10k$, $C = 82n$), High ($f_c = 1$ kHz, $R = 10k$, $C = 15n$).

Block 6: Sawtooth Sweep Generator & VCO (06_Sawtooth_VCO.asc)

- **Topology:** TL072 Integrator ($C_{time} = 10n..100n$, $R_{charge} = 100k$, $I_{charge} = 50 \mu A$) + TL072 Schmitt Trigger + 2N3904 Reset BJT. Produces a 0V to 5V linear ramp tuning LO from 20 kHz to 50 kHz.

3. Comprehensive Simulation Suite (Implementation & Directives)

Sim 1: AC Frequency Response & Stability Analysis

Goal & Description: Validates resonant frequency $f_0 = 25$ kHz $\pm$ 100 Hz, BW = 200 Hz $\pm$ 25 Hz, and verifies unconditional stability (monotonic phase decrease).

```
.ac dec 200 10k 50k
.meas AC f_center MAX mag(V(IF_out_2))
.meas AC f_low WHEN mag(V(IF_out_2))=f_center/sqrt(2) FALL=1
.meas AC f_high WHEN mag(V(IF_out_2))=f_center/sqrt(2) RISE=1
.meas AC bw PARAM (f_high - f_low)
```

Sim 2: Component Tolerance & Monte Carlo Analysis

Goal & Description: 100-run statistical sweep ensuring >95% of runs remain within 25 kHz $\pm$ 250 Hz (1.0%) center frequency spread with 1% resistors and 5% caps.

```
.param R3_val = {mc(796k, 0.01)}
.param R4_val = {mc(6.34k, 0.01)}
.param C3_val = {mc(1n, 0.05)}
.param C4_val = {mc(1n, 0.05)}
.step param run 1 100 1
```

Sim 3: Worst-Case Sensitivity Analysis

Goal & Description: Evaluates maximum frequency error bounding box (Δf_{max}) across all binary tolerance corner permutations.

```
.param R3_wc = {wc(796k, 0.01, 1)}
.param R5_wc = {wc(796k, 0.01, 2)}
.param C3_wc = {wc(1n, 0.05, 3)}
.param C4_wc = {wc(1n, 0.05, 4)}
.step param run 1 16 1
```

Sim 4: Thermal Drift Analysis

Goal & Description: Quantifies frequency shift across temperature caused by semiconductor V_{be} tempco (-2 mV/°C), op-amp offset drift, and resistor TCR (< 50 Hz drift).

```
.model RES_PRECISION R (tc1=50e-6) ; 50 ppm/°C metal film
.step temp 0 70 10
```

Sim 5: Mixer Intermodulation Distortion & Linearity (FFT)

Goal & Description: FFT on V(mix_out). Measures mixing products (25.0, 25.2 kHz) and 3rd-order intermod products (24.8, 25.4 kHz). Verifies SFDR $\geq$ 45 dBc.

```
* Two-Tone Input: 5.0 kHz + 5.2 kHz (100 mVpk each); LO = 20.0 kHz
.tran 0 20m 10m 100n
```

Sim 6: Master Dynamic Multi-Tone Sweep

Goal & Description: Plots V(env_out) vs V(ramp) in simulated X-Y display mode. Confirms 3 distinct, symmetric spectral peaks without asymmetrical ringing tails.

```
* Three-tone RF: 4.0 kHz + 7.0 kHz + 12.0 kHz; Sweeping LO: 20 kHz to 40 kHz
.tran 0 100m 0 1u
```

4. Summary of Simulation Deliverables

#	Schematic File	Simulation Type	Key Directive	Target Deliverable
1	03_IF_Filter_Bank.asc	AC Response	.ac dec 200 10k 50k	f0 = 25 kHz, BW = 200 Hz, Q = 125, Stable
2	03_IF_Filter_Bank.asc	Monte Carlo	.step param run 1 100 1	$\Delta f_0 < \pm 250$ Hz across 100 runs (1% R)
3	03_IF_Filter_Bank.asc	Temperature	.step temp 0 70 10	$\Delta f_0 < 50$ Hz over $\Delta T = 40$ °C
4	02_Gilbert_Mixer.asc	Linearity / FFT	.tran 0 20m 10m 100n	SFDR $\geq$ 45 dBc, conversion gain
5	06_Sawtooth_VCO.asc	Ramp Linearity	.tran 0 50m 0 1u	0V to 5V linear ramp, flyback < 0.5 ms
6	SpectrumAnalyzer_Master.asc	Master Sweep	.tran 0 100m 0 1u	Full 3-tone spectrum in X-Y display mode